

Flip Flop Exercise

- 1) Draw the two SR Latch Circuit with 2 input(S & R)
- 2) Draw the two D Latch Circuit with 2 input(C & D)