

NAND and NOR

Perform the following implementation in a multi layer digital logic design (i.e. without opening up the brackets). Use CEDAR simulation to demonstrate that both designs are equivalent.

NAND implementation (F1-NAND)

$$F1 = (BD + B'C)A + B'C'$$

NOR Implementation (F2-NOR)

$$F2 = \{[(A+B)(A'+C)]+D\}(B'+C')$$