

# Digital Logic Design (CSNB163)

Module 12


# Combinational Vs. Sequential Logic Circuit

---

- In Module 9, 10, 11, you have been introduced to examples of combinational logic circuits whereby the outputs are entirely dependent on the **current inputs**.
- The following topics will be on sequential logic circuits, whereby in addition to the external inputs, the circuits also receives data from the the **present state of the storage elements**.
 
# Sequential Logic Circuit

- A sequential circuit consists of a combinational circuit with a **storage elements** connected to form a **feedback path**.
- The storage elements are devices capable of **storing binary information**.
- The binary information that stored in these elements **at any given time** defines the state of the sequential circuit at that time.




# Sequential Logic Circuit (cont.)

---


- Two main types of sequential circuit (where classification depends on the timing of signals):
  - A **synchronous** sequential circuit - a system whose behavior can be defined from the knowledge of its signals at **discrete instants of time**. Synchronization is achieved by a timing device called a **clock generator** which provide a clock signal having the form of a periodic train of clock pulses.
  - An **asynchronous** sequential circuit - a system whose behavior depends upon the input signals at **any instant of time** and the order in which the inputs change. There is **no clock** in this circuit and thus, the signal changes are run freely and depend on signal order in the circuit.
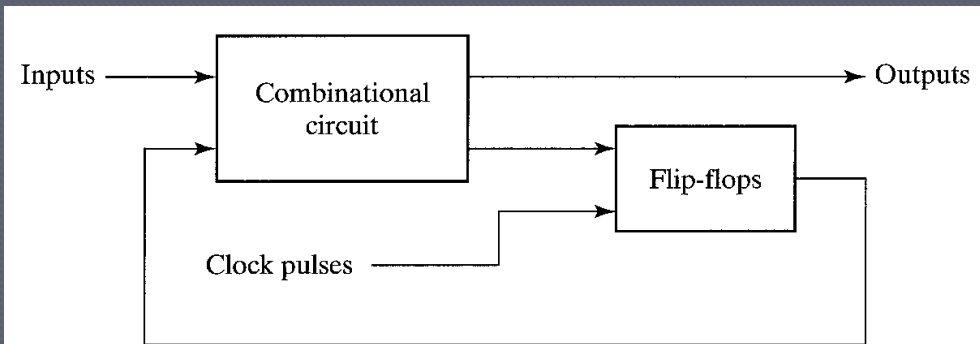
# Flip-Flops

- The storage element in synchronous sequential circuit is called **flip-flop** :- a binary **storage device** capable of storing **one bit binary data**.
- A flip-flop receives inputs from the **combinational circuit** and from a **clock**.
- Flip-flops are constructed by **latches**.
- Flip-flop **remains its state** as long as it is **powered**.



(a) Block diagram

 

(b) Timing diagram of clock pulses


# Latches

---

- Latches are device that constructed by basic **logic gates** to store **a single bit** of binary data.
- **Flip-flops** are constructed by **latches**.
- **Function table** (or **characteristics table**) describes the properties or characteristics of latches / flip flops.
- There are various kind of latches, we shall cover:
  - **SR latch**
  - **$\overline{S}\overline{R}$  latch**
  - **SR latch with control input**
  - **D latch**
 
# SR Latch

- The SR latch is a circuit with 2 cross-coupled NOR gates. It has 2 inputs labeled S (Set) and R (Reset).



(a) Logic diagram

$S$	$R$	$Q$	$Q'$	
1	0	1	0	(after $S = 1, R = 0$ )
0	0	1	0	
0	1	0	1	(after $S = 0, R = 1$ )
0	0	0	1	
1	1	0	0	

(b) Function table



# SR Latch (cont.)


## ○ Characteristics:

- **Set State: when output  $Q = 1$  and  $Q' = 0$  ( $S=1, R=0$ )**
- **Reset State: when output  $Q = 0, Q' = 1$  ( $S=0, R=1$ )**
- Output  $Q$  and  $Q'$  is **complement** to each other.
- Under normal condition, both inputs of SR latch remain at **0** ( $S = 0$  &  $R = 0$ ), unless the state has to be change.
- If both inputs are **1** ( $S = 1$  &  $R = 1$ ), the output is  $Q = 0, Q' = 0$  which regards as an **undefined state**.
- Before any **state change**, the both SR latch inputs **must be set to 0** (to avoid the occurrence of undefined state).
- After set or reset state, the output will **remain unchanged** even though the input is removed (return to 0).


 
# $\overline{S}\overline{R}$ Latch

- The characteristics of  $\overline{S}\overline{R}$  latch are the **opposite** to SR latch (some references may refer them with the same name, does not matter...)
- It is a circuit with 2 cross-coupled NAND gates instead of 2 NOR gates.



(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1


(after  $S = 1, R = 0$ )

(after  $S = 0, R = 1$ )

(b) Function table
 
# SR Latch with Control Input

- The operation of basic SR latch can be modified to determine when the state of the latch can be changed by adding a control input.



(a) Logic diagram

C	S	R	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table


# SR Latch with Control Input (cont.)

---

- The control  $C$  acts like an input to the other 2 inputs. The circuit functions only when  $C = 1$  and remain the output as it is when  $C = 0$ .
- Characteristics:
  - **Set State:** when output  $Q = 1$  and  $Q' = 0$  ( $C=1, S=1, R=0$ )
  - **Reset State:** when output  $Q = 0, Q' = 1$  ( $C=1, S=0, R=1$ )
  - **Remain unchanged:**  $C = 0$
  - **An indeterminate condition occurs when all 3 inputs are equal to 1.**
 
# D Latch


- D (**Delay**) latch is designed **to eliminate the indeterminate condition in the SR latch.**
- D latch ensures that inputs S and R are never equal to 1 at the same time.
- $S = D, R = \overline{D}$ , thus  **$R \neq S$ .**




C	D	Next state of Q
0	X	No change
1	0	$Q = 0$ ; Reset state
1	1	$Q = 1$ ; Set state
 
# Graphical Symbol of Latches


- The graphical symbol for various latches is shown below.
- The bubble indicates the complement input/output.



SR latch

 

$\overline{S}\overline{R}$  latch

 

D latch

# Triggering Flip – Flops

- The state of a flip-flop is switched by a momentary change in **clock signal** that acts as a control input that triggers.
- 3 types of trigger signal:
  - Positive level trigger
  - Positive edge trigger
  - Negative edge trigger



(a) Response to positive level



(b) Positive-edge response



(c) Negative-edge response

# Triggering Flip – Flops (cont.)

---

## ⊙ Positive level trigger:

- Allows changes in the output when the input changes while the clock pulse stays at logic '1'
- Problem: **if more than 1 changes** happen at the input signal and **output will keep on changing** following the input signal as long as the trigger signal still stay in positive level, thus causing confusion


## ⊙ Edge trigger:

- **Preferred solution** to avoid confusion.
- Edge trigger can be **positive** (during '0' to '1' transition) or **negative** (during '1' to '0' transition)
- In this Module, we use different D-flip flop implementations to demonstrate the example of positive and negative edge flip flops.


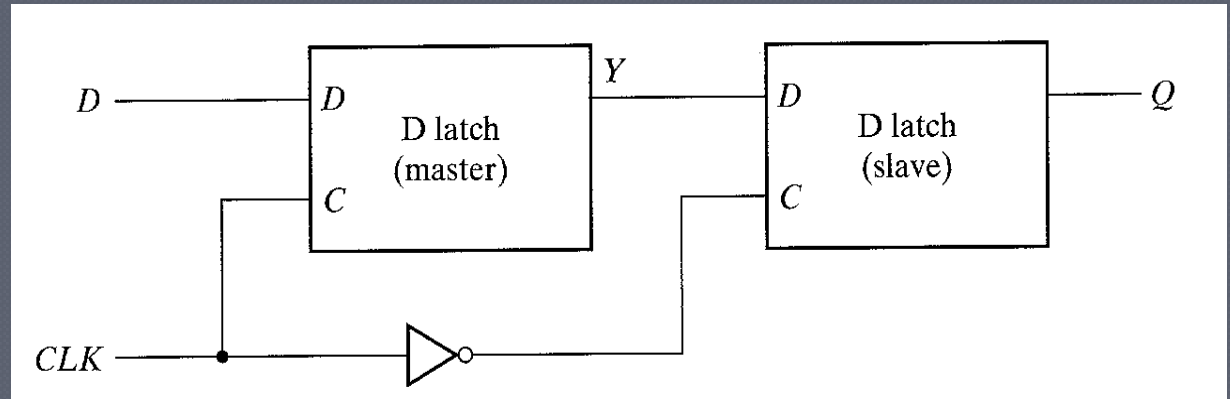
# Negative Edge Triggered D Flip-Flop using 2 D-latches

- D flip-flop can be constructed with **two D-latches**.




- Properties:
  - When **CLK is 1**, **master D latch is enabled** but **slave D latch is disabled**. **Input (D)** will be transferred to **Y**.
  - When **CLK is 0**, **slave D latch is enabled** but **master D latch is disabled**. **Data (Y)** will be transferred to **Q**.
  - Thus, changes in output occur only **during transition from '1' to '0'** (negative edge trigger D flip-flop).

# Positive Edge Triggered D Flip-Flop using 3 SR-latches

- D flip flop can also be constructed using three NAND coupled SR latches.


- Properties:

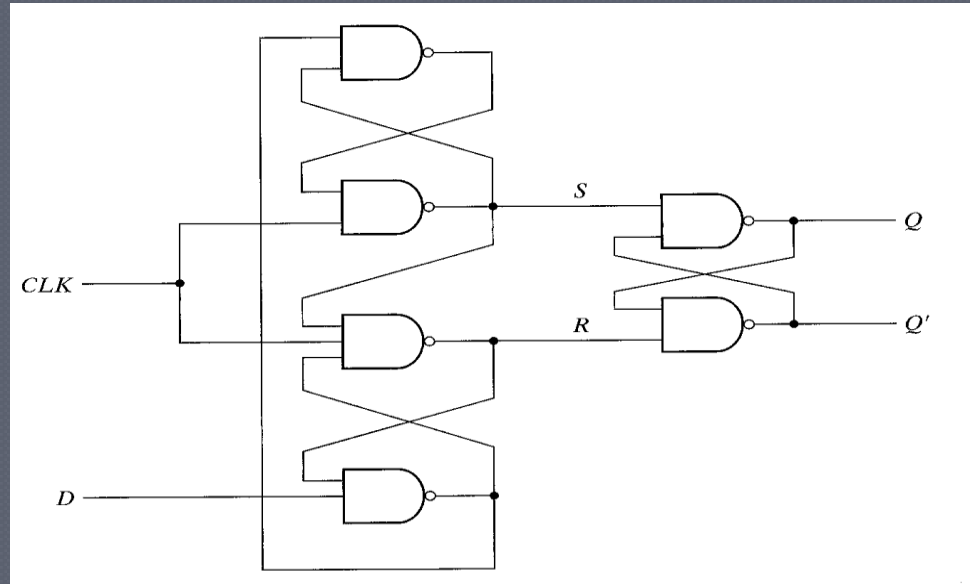- When CLK is 0, (regardless of D) both S and R remains 1, thus Q and Q' remains at the previous state (no changes)
- When CLK is 1, if D = 1, then S = 0, R = 1, thus Q = 1, Q' = 0
- When CLK is 1, if D = 0, then S = 1, R = 0, thus Q = 0, Q' = 1
- Thus, changes in output occur only **during transition from '0' to '1'** (positive edge trigger D flip-flop).



 
# Graphical Symbol of Flip Flops

- The graphical symbol for different edge triggered D flip-flops is shown below.
- The bubble indicates the complement input/output.
- The arrowhead symbol in front of C indicates that the flip-flop responds to edge triggering



+ edge triggered D flip flop

 

- edge triggered D flip flop

# Digital Logic Design (CSNB163)

End of Module 12