

# Digital Logic Design (CSNB163)

Module 3

# Binary Logic

- Binary logic consists of :

- logic variables**

- designated by alphabet letters, e.g. A, B, C... x, y, z, etc.
    - have ONLY 2 possible values: **1** or **0**

$A + B = Y$

- logic operators**

- 3 basic logical operators representing 3 basic logical operations: **AND**, **OR** and **NOT**

- The overall equation made up a **Boolean Equation**

# Logic Gates

---

- Logic gates are **electronic circuits** that **operate on one or more binary input signals** to produce **a binary output signal**.
- Each logic gate represents a single processing unit that **performs binary logic operations**

# Truth Tables

---

- Truth table is a **table of all possible combinations** of the input binary variables
- If there are  **$n$**  input variables, there are in total  **$2^n$**  possible combination
- Truth tables show the relationship between the **input binary values** that the **output binary result of the operation**

# Timing Diagram

---


- Timing diagram is a **graphical representation** that describe the **relationship** between **input(s)** and **output signals** in a digital circuit system.
- In actual implementation, the input and output signals are **electrical signals** that can be categorized into binary logic state of 1 or 0 based the defined range of voltages associated with each state.
- Input signal can either **static** (e.g. logic state 0 if grounded) or **dynamic** (e.g. if received input from flip flops)

# Binary Logic Operation (AND)

- Symbol dot or none
- Boolean Equation  
 $A \cdot B = Y$  or  $AB = Y$
- Output variable is 1 if **all** input variables is 1
- Logic Gate

- Truth table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 


# Binary Logic Operation (AND)

- Boolean Equation

$$A \cdot B \cdot C = Y$$

- Logic Gate

 


- Truth table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1
 
# Binary Logic Operation (OR)

- Symbol plus
- Boolean Equation  
 $A + B = Y$
- Output variable is 1 if **any** input variables is 1
- Logic Gate



- Truth table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1




# Binary Logic Operation (OR)

- Boolean Equation

$$A + B + C = Y$$

- Logic Gate

 

- Truth table


A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

# Binary Logic Operation (NOT)

- Symbol prime or overbar  
 $\overline{A} = Y$  or  $A' = Y$
- Output variable is **always opposite** of input variable
- Logic Gate


- Truth table

A	Y
0	1
1	0

 
 
# Binary Logic Operation (NAND)

- A combination of **AND** operation **followed by NOT** operation
- Symbol  
 $A \cdot B = Y$  or  $\overline{AB} = Y$
- Logic Gate



- Truth table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

# Binary Logic Operation (NOR)


- A combination of **OR** operation **followed by NOT** operation

- Symbol  
 $A + B = Y$

- Logic Gate

- Truth table

<b>A</b>	<b>B</b>	<b>Y</b>
0	0	1
0	1	0
1	0	0
1	1	0

 


# Binary Logic Operation (XOR)

- Exclusive OR (XOR)
- Symbol  $\oplus$
- Boolean Expression  
 $AB' + A'B = Y$
- Logic Gate

- Truth table

<b>A</b>	<b>B</b>	<b>Y</b>
0	0	0
0	1	1
1	0	1
1	1	0

 


# Binary Logic Operation (XNOR)

- Exclusive NOR (XNOR)
- Symbol  $(A \oplus B)'$
- Boolean Expression  
 $AB + A'B' = Y$
- Logic Gate

- Truth table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

 

# NAND and NOR gates

---

- Digital circuits are more frequently constructed with NAND or NOR gates rather than with AND or OR gates.
- The main reason behind this is that NAND and NOR gates are easier to fabricate with electronic components.

# XOR gates

---

- Exclusive OR gates are often used for error detection and correction purposes.
- This is done by using XOR gates in building the parity generator and checker digital logic circuits.



# Digital Logic Design (CSNB163)

End of Module 3