

# Digital Logic Design (CSNB163)

Module 9

# Categories of Logic Circuit

---

- Digital logic circuits can be categorized based on the nature of their inputs either:
  - **Combinational logic circuit**

It consists of logic gates whose outputs at any time are determined from the present combination of inputs. It can perform an operation that can be specified logically by a set of Boolean functions. (The subsequent modules are based on combinational logic circuit)
  - **Sequential logic circuit**

It employs storage elements in addition to logic gates. Their outputs are a function of the inputs and the state of the storage elements. (the last module on flip-flops & latches is on sequential logic circuits)

# Construction of Combinational Logic Circuit

---

- Combinational logic circuits can be constructed based on the following steps:
  1. Derive the **Truth Table** (to perform the given function)
  2. Derive the **Karnaugh Map** (from the truth table)
  3. Derive the **simplified Boolean expression(s)** (from the K-map(s))
  4. Draw the **circuit diagram(s)** (to implement the simplified Boolean expression(s))

# Binary Adder

---

- Binary adder performs the addition of two or more binary digits.
- Two types of binary adder:
  - **Half adder**

The **input** is **two** binary variables ( **$a$** ,  **$b$** )

The **output** is **two** binary variables ( **$sum$** ,  **$c_{out}$**  being the output carry)
  - **Full adder**

The input is **three** binary variables ( **$a$** ,  **$b$** ,  **$c_{in}$**  being the input carry)

The **output** is **two** binary variables ( **$sum$** ,  **$c_{out}$**  being the output carry)

# Half Adder

- This circuit needs:

- 2 inputs; augend ( $a$ ) and addend ( $b$ )
- 2 outputs; sum ( $sum$ ) and output carry ( $c_{out}$ ).

- Truth table:


$a$	$b$	$sum$	$c_{out}$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$sum = a'b + ab'$$

$$c_{out} = ab$$


# Half Adder (cont.)

## ● Circuit diagram:

 

$$c_{out} = ab$$

$$sum = a'b + ab'$$

 

# Full Adder

## ⊙ This circuit needs:

- 3 inputs; augend ( $a$ ), addend ( $b$ ) and input carry ( $c_{in}$ )
- 2 outputs; sum ( $sum$ ) and output carry ( $c_{out}$ ).

## ⊙ Truth table:

$a$	$b$	$c_{in}$	$sum$	$c_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$sum = a'b'c_{in} + a'bc_{in}' + ab'c_{in}' + abc_{in}$$

$$c_{out} = a'bc_{in} + ab'c_{in} + abc_{in}' + abc_{in}$$

# Full Adder (cont.)

- Sum of minterms (derived from Truth Table)

$$\begin{aligned} \text{sum} = & a'b'c_{in} + a'bc_{in}' \\ & + ab'c_{in}' + abc_{in} \end{aligned}$$

$$\begin{aligned} c_{out} = & a'bc_{in} + ab'c_{in} \\ & + abc_{in}' + abc_{in} \end{aligned}$$

- Karnaugh map:

sum

		bc <sub>in</sub>			
		00	01	11	10
a	0		1		1
	1	1		1	

c<sub>out</sub>

		bc <sub>in</sub>				
		00	01	11	10	Group1: bc <sub>in</sub>
a	0			1		
	1		1	1	1	Group2: ac <sub>in</sub> Group3: ab

- Simplified Boolean expressions:


$$\begin{aligned} \text{sum} = & a'b'c_{in} + a'bc_{in}' \\ & + ab'c_{in}' + abc_{in} \end{aligned}$$

$$\begin{aligned} c_{out} = & bc_{in} + ac_{in} \\ & + ab \end{aligned}$$




# Full Adder (cont.)

## ● Circuit diagram:

 

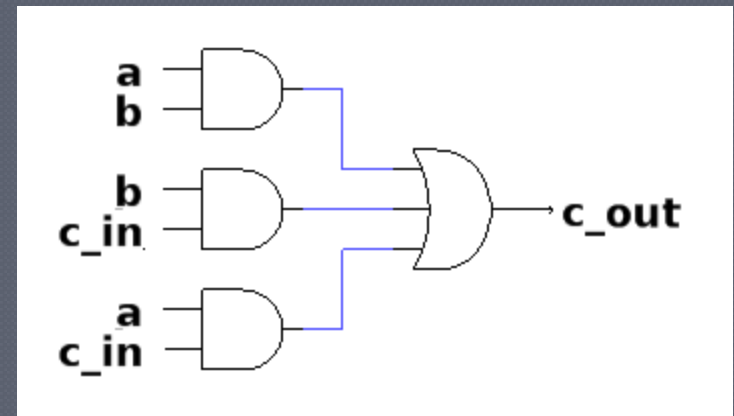
$$sum = a'b'c_{in} + a'bc_{in}' + ab'c_{in}' + abc_{in}$$



$$c_{out} = bc_{in} + ac_{in} + ab$$
 
# Constructing a Full Adder using Half Adders

- A full adder can also be implemented by using two half adders and an OR gate.
- Recaps half adder consists of **AND** and **XOR** operation:



$$c_{out} = ab$$

$$sum = a'b + ab'$$

- Thus, in order to construct a full adder using half adders, we need to represent the Boolean expressions of a full adder using AND and XOR operations.

# Constructing a Full Adder using Half Adders (cont.)

## Sum Boolean expression of a full adder:


$$sum = a'b'c_{in} + a'bc_{in}' + ab'c_{in}' + abc_{in}$$

$$sum = c_{in}(a'b' + ab) + c_{in}'(a'b + ab')$$

$$sum = c_{in}(a \oplus b)' + c_{in}'(a \oplus b)$$

$$sum = (a \oplus b) \oplus c$$
 
## $C_{out}$ Boolean expression of a full adder:



$$C_{out} = a'bc_{in} + ab'c_{in} + abc_{in}' + abc_{in}$$


$$C_{out} = ab + a'bc_{in} + ab'c_{in}$$

$$C_{out} = ab + c_{in}(a'b + ab')$$

$$C_{out} = ab + c_{in}(a \oplus b)$$

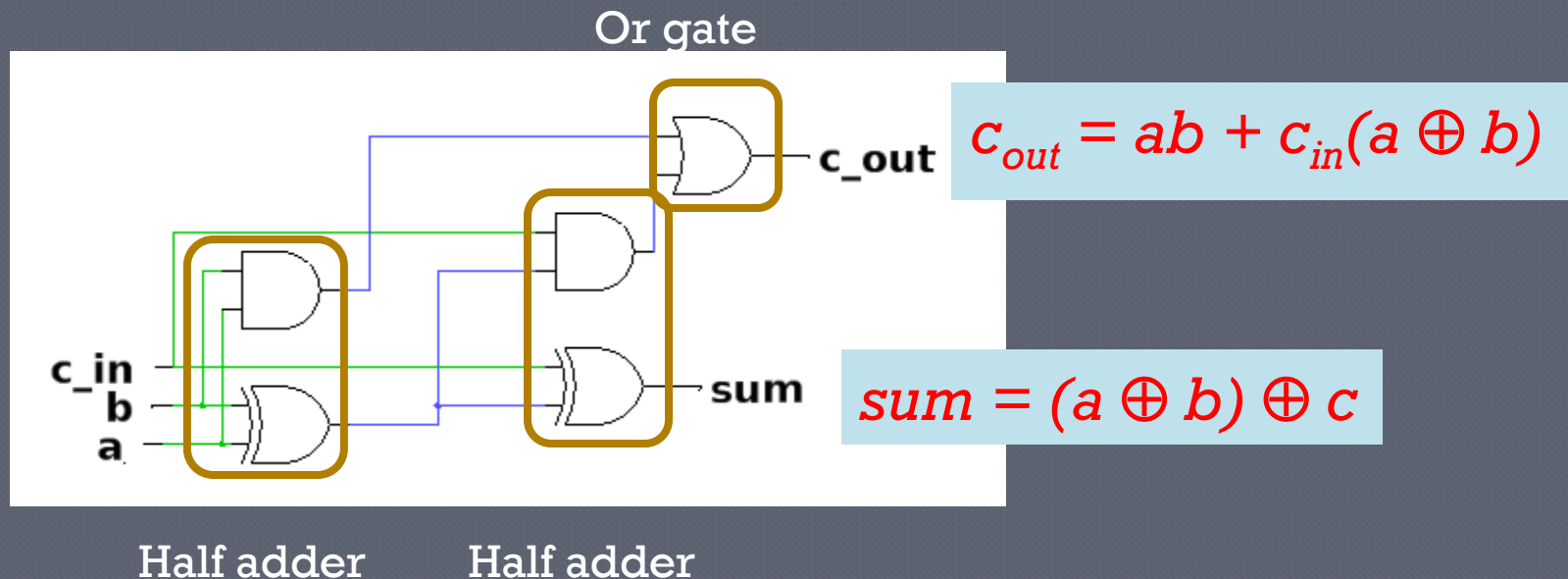
# Constructing a Full Adder using Half Adders (cont.)

- Circuit diagram of a full adder (which is made up of 2 half adders and 1 OR gate):


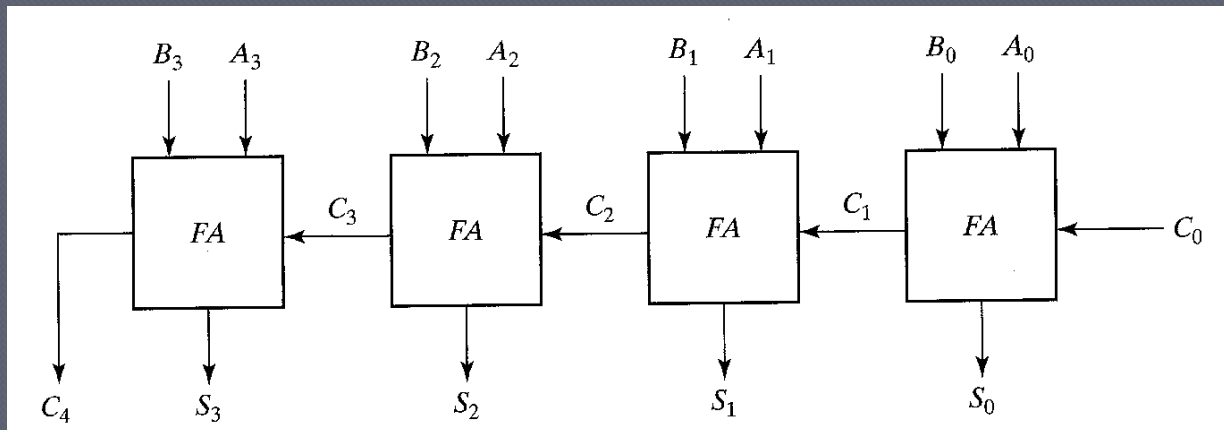
# $n$ -bits Cascaded Binary Adder

- **An  $n$ -bits binary adder** is capable of performing addition of binary digits up to  **$n$  bits**.
- **An  $n$ -bits binary adder** requires for  **$n$  full adders** setup in a **cascaded manner**.
- E.g. 4-bits binary adder with 4 full adders:



## $n$ -bits Cascaded Binary Adder (cont.)

- A 4-bits cascaded binary adder is capable of performing 4 bits binary operation as follows:

$i$	4	3	2	1	0
Input Carry ( $c_i$ )	-	1	1	0	0
Augend ( $a_i$ )	-	1	1	1	0
Addend ( $b_i$ )	-	1	0	1	1
Sum ( $sum$ )	-	1	0	0	1
Output carry ( $c_{i+1}$ )	1	1	1	1	0

E.g. Augend = 1110

E.g. Addend = 1011

Sum = 1001 with  
output carry  $c_4 = 1$

# $n$ -bits Cascaded Binary Adder (cont.)

## ○ Properties:

- The bits are added with full adder, **starting** from the **least significant** position to form the sum bit and carry bit then proceeds to the higher significant bits.
- The initial input carry  $c_0$  must be **0**.
- The **output carry  $c_{i+1}$**  is **transferred** into the **input carry  $c_i$**  of the full adder that adds the higher significant bits.
- The sum bits are generated starting from the least significant bit and are available **as soon as the corresponding previous carry bit is generated**.
- Thus, **all the carries must be generated for the correct sum bits to appear at the outputs**.
- If each full adder has a delay of  $t_{delay}$ ,

$$\text{Total delay} = n \times t_{delay}$$

# Digital Logic Design (CSNB163)

End of Module 9